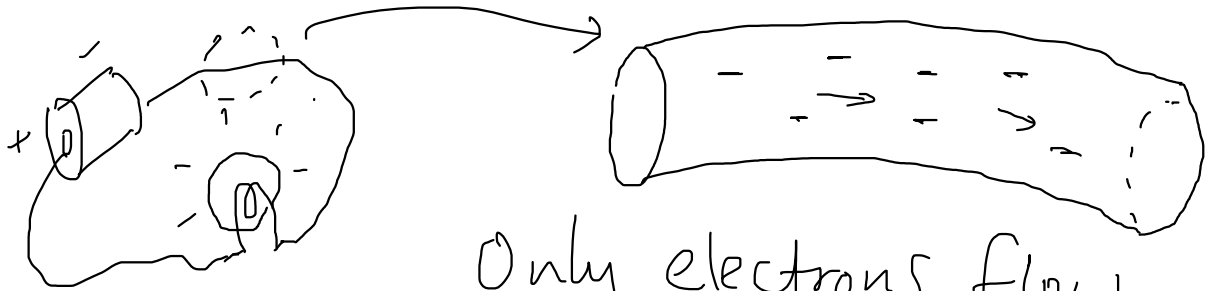


Electric Current

Dr K M Hock




Only electrons flow.
The rest of the atoms don't.
(10000 x heavier)

→ Current in wires :

Negative electrons from -ve to +ve poles.

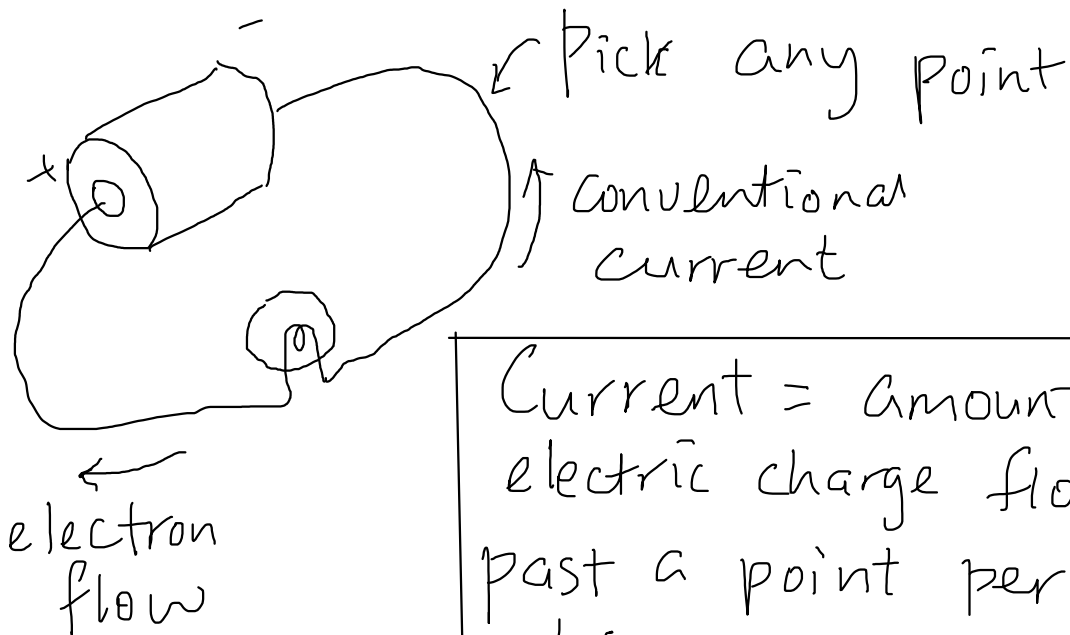
"Conventional Current" - imaginary/
equivalent +ve charges from +ve
to -ve poles.



Current = amount of electric charge flowing past a point per unit time.


Charge, Coulomb

Dr K M Hock

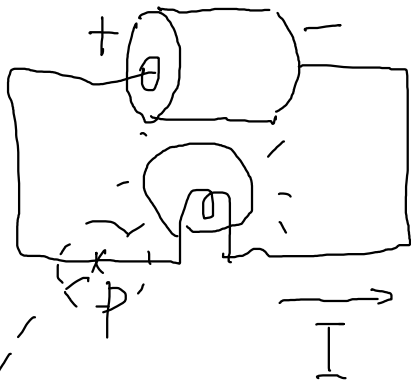

If I just say a current flows to the right, it means a conventional current.

So electrons flow to the left!

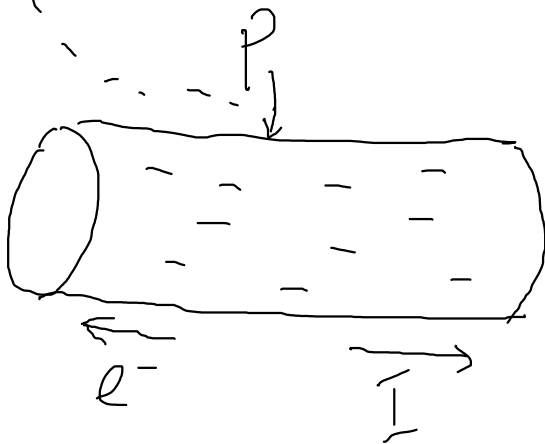

e.g. Current $I = 1$ Ampere (A)

means 1 Coulomb (C) of charge flows past a point (e.g. P) in 1 s.

But how many electrons actually flow past P?


1 electron's charge, $e = 1.6 \times 10^{-19} \text{ C}$.

$$\text{No. of electrons in } 1 \text{ C} = \frac{1 \text{ C}}{1.6 \times 10^{-19} \text{ C}} = 6.25 \times 10^{18}$$

\therefore 1 A of current $\rightarrow 6.25 \times 10^{18}$ electrons in 1 s.

Electric Current 2

Dr K M Hock

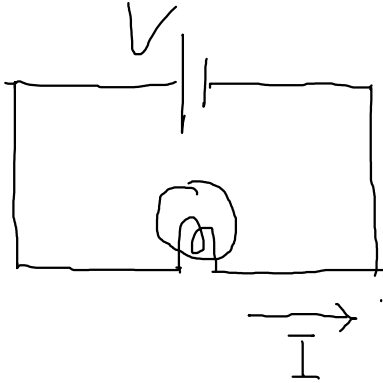

$$\text{Current} = \frac{\text{Charge}}{\text{time}}$$

$$I = \frac{Q}{t}$$

Charge Q flows past a point in time t .

e.g. 2A of current flows through a light bulb. How much charge flows through the bulb in 1 min.


$$Q = It = 2A \times 60s = 120C$$

e.g. How many electrons flow through?
 $e = 1.6 \times 10^{-19}C$

$$\text{no. of } e^- = \frac{Q}{e} = \frac{120}{1.6 \times 10^{-19}} = \underline{\hspace{2cm}}$$

Potential Difference

Dr K M Hock

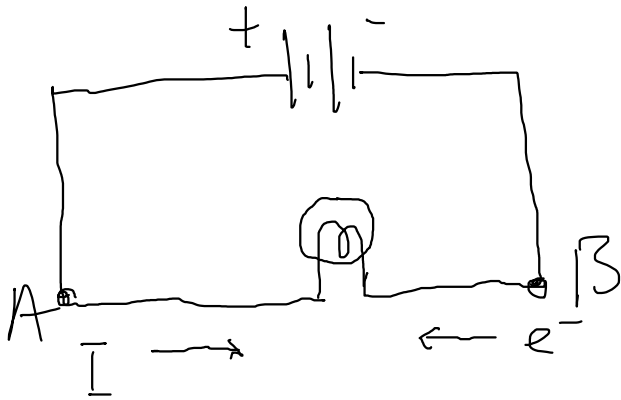

Battery must do work to push e^- as they knock against atoms.

e.g. 2 J of work is done to move 1 C of charge from A to B.

Say: Potential difference between A and B is 2 volts (V).

Potential difference between 2 points is the work done to move unit charge from one point to the other point.

$$p.d \rightarrow V = \frac{W}{Q}$$

- work
- charge

Unit = volt (V)

$$1V = 1J/C$$

Potential Difference 2

Dr K M Hock



e.g. - resistance in battery
and wires can be ignored.

How much work is needed to bring 5C from A to B?


$$V = \frac{W}{Q}$$

$$W = QV = 5\text{C} \times 10\text{V} = 50\text{J}$$

What happens to this energy? \rightarrow Light, heat

How much work is done to move an electron from C to D?
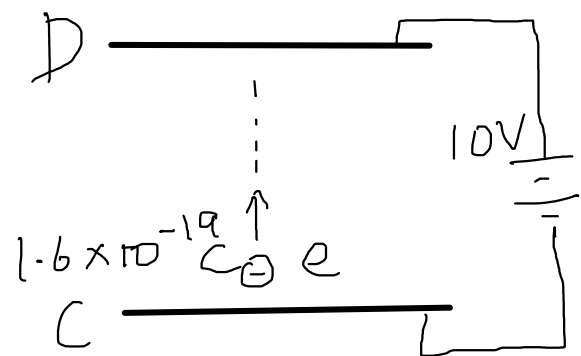
$$\begin{aligned} W &= QV \\ &= 1.6 \times 10^{-19} \times 10 \\ &= 1.6 \times 10^{-18} \text{ J} \end{aligned}$$



What happens to this energy?

\rightarrow KE of e^-

Electric Power

Dr K M Hock



e.g. how much charge goes thru' the bulb in 5s?

how much work is done?

What is the power?

Charge $Q = It = 1 \times 5 = 5C$

Work $W = QV = 5C \times 10V = 50J$

Power $P = \frac{W}{t} = \frac{50J}{5s} = 10W$

$$\downarrow$$

$$P = \frac{W}{t} = \frac{QV}{t} = IV$$

Can also do $P = IV = 1A \times 10V = 10W$

Ohm's law $V = IR$ - resistance

$$\therefore \boxed{P = IV = I^2 R}$$

define resistance and the ohm
recall and solve problems using $V = IR$

Ohm's law

Dr K M Hock



e.g. - Find resistance of the light bulb.

$$V = IR$$


$$R = \frac{V}{I} = \frac{10V}{1A} = 10\Omega$$

e.g. find internal resistance of cell.

Total resistance in circuit

$$R_T = \frac{V}{I} = \frac{10V}{1A} = 10\Omega$$









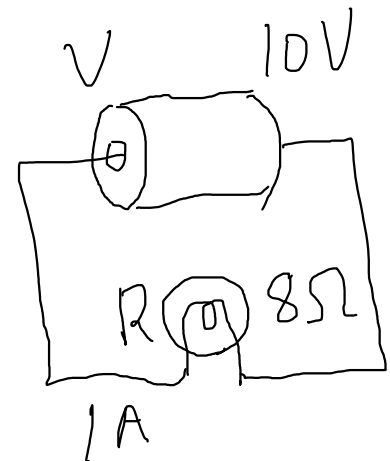
$$\text{Internal resistance} = R_T - R = 10 - 8\Omega$$



sketch and explain the I-V characteristics of a metal conductor at constant temperature, a semiconductor diode and a filament lamp

I-V Characteristics




Dr K M Hock

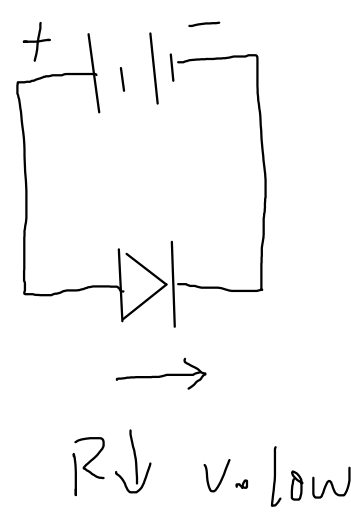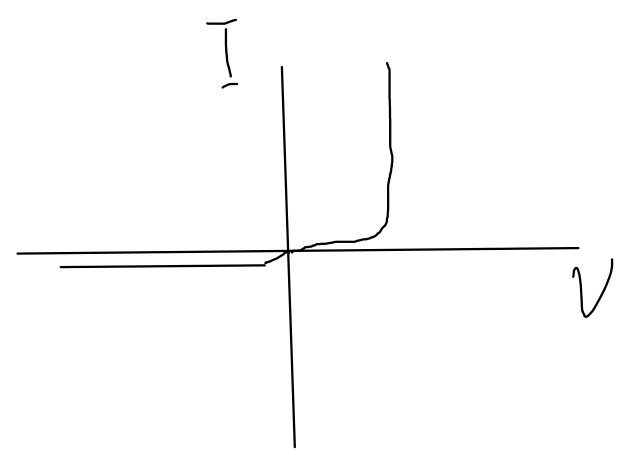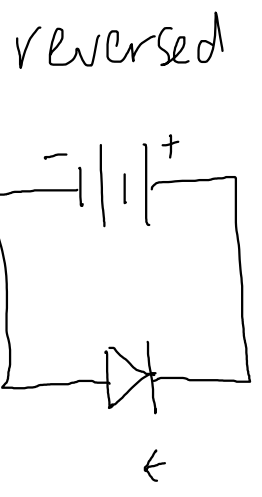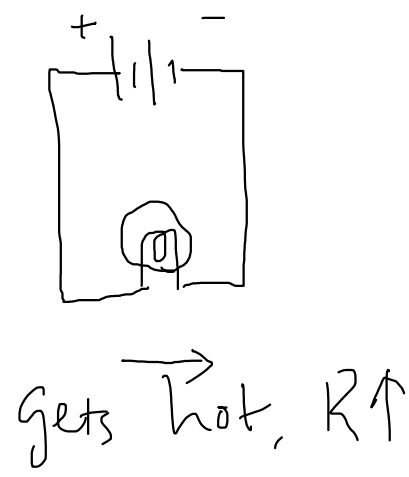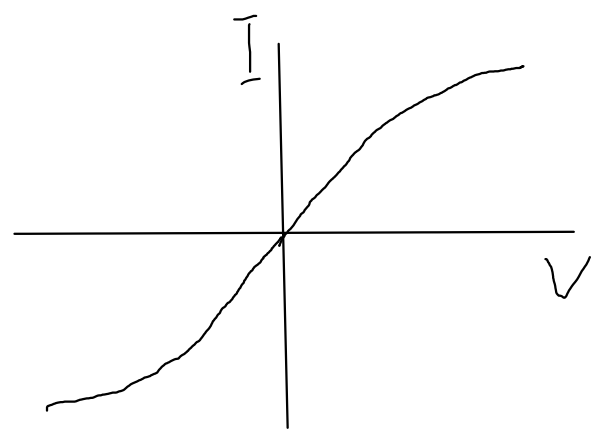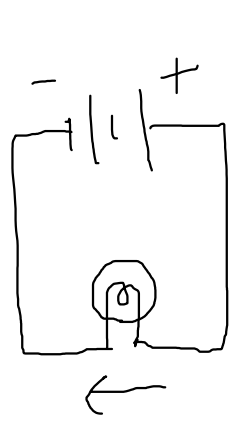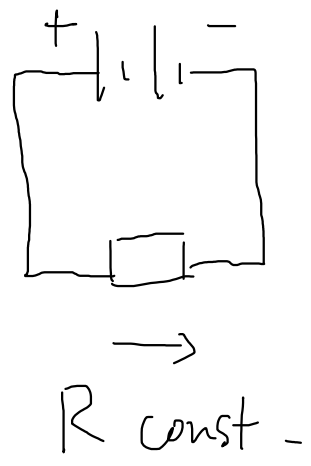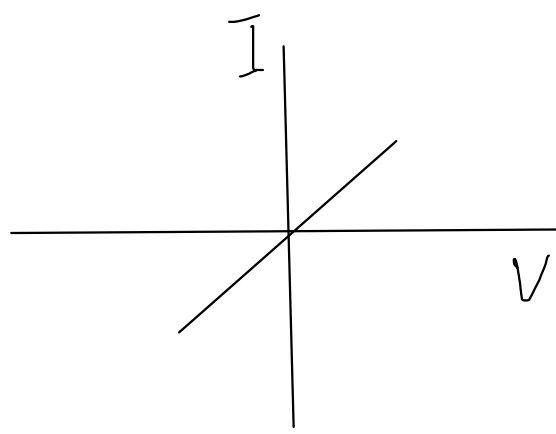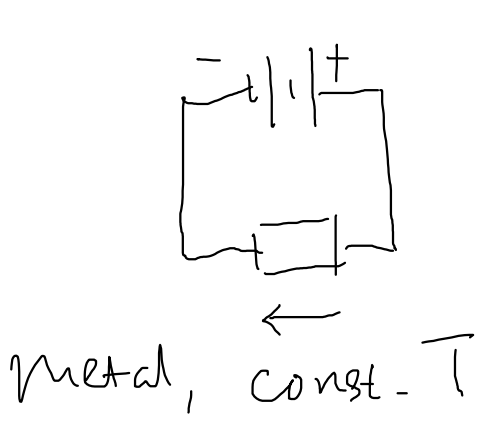

cannot flow
 $R \uparrow$ v. large


Thermistor

Dr K M Hock

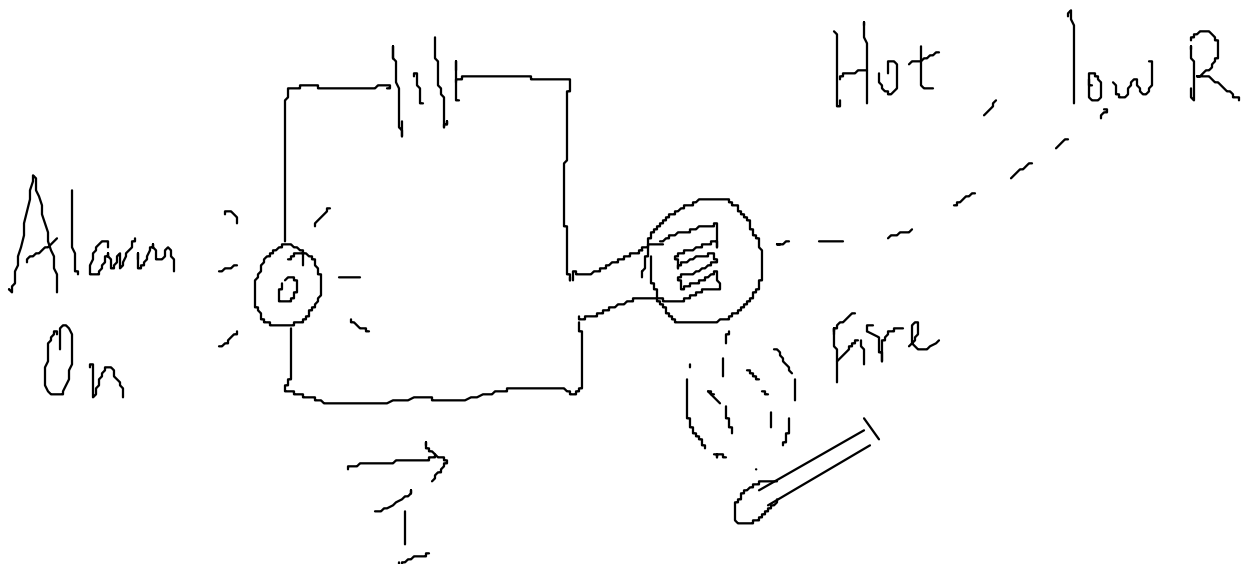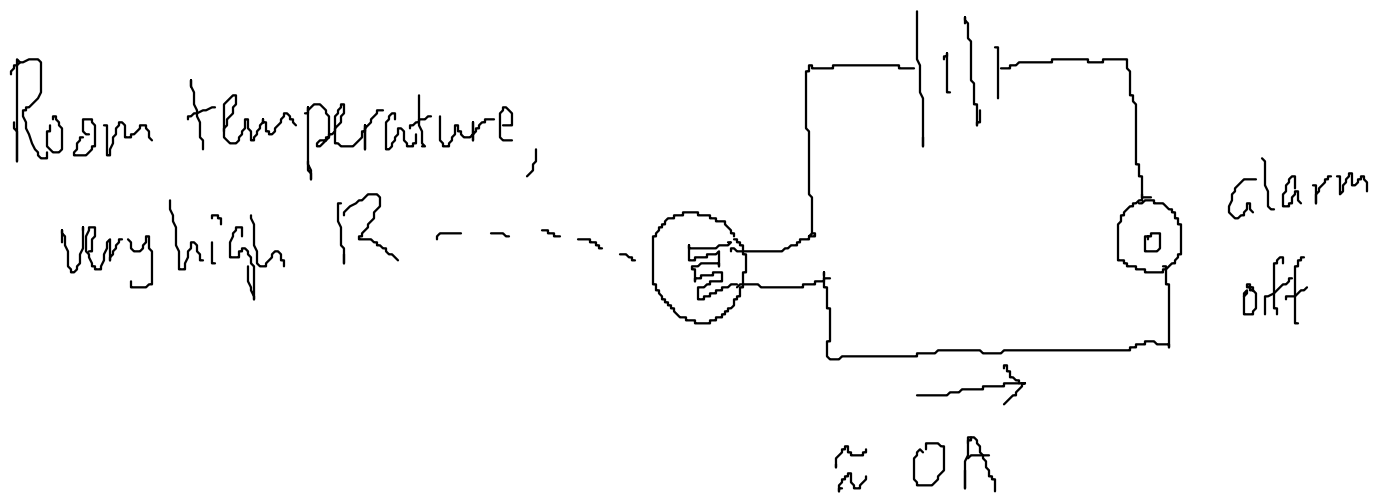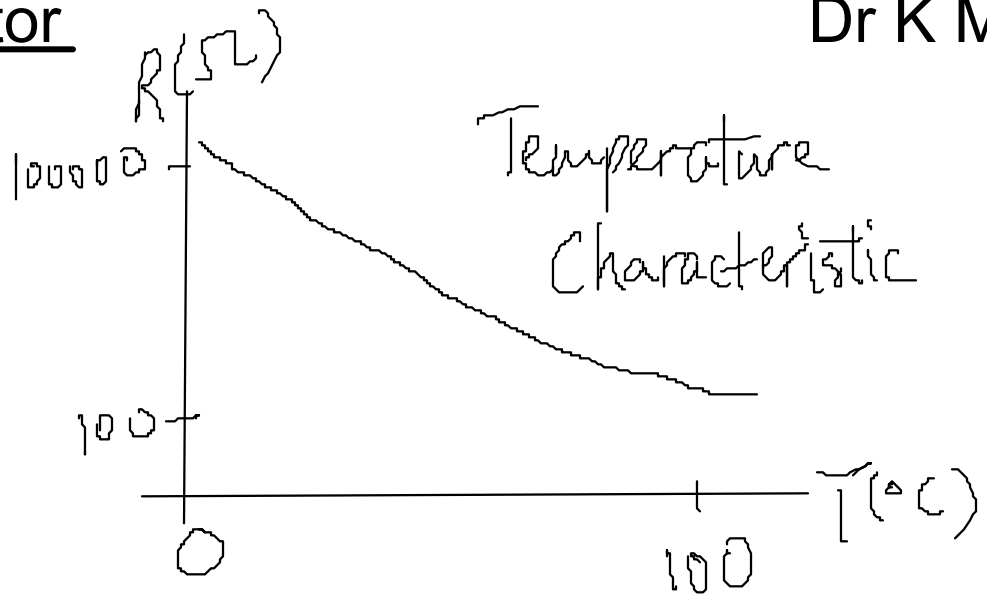


Resistivity

Dr K M Hock

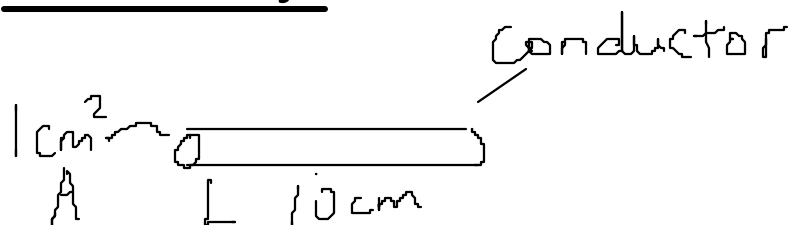



$$0.1 \Omega$$

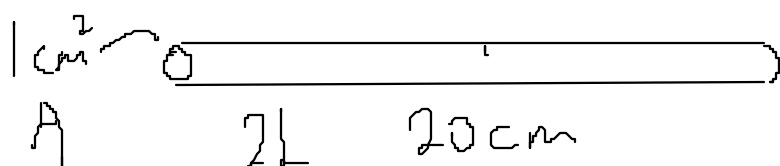

$$0.1 \Omega \times 2$$

Resistance proportional to length

$$R \propto L$$

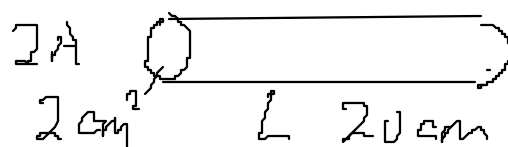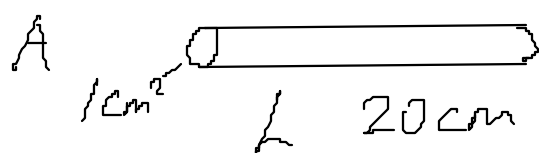

$$R: 0.1 \Omega$$

$$\frac{1}{2} \times 0.1 \Omega$$

Resistance proportional to $\frac{1}{\text{area}}$

$$R \propto \frac{1}{A}$$

constant

Combining:

$$R = \rho \frac{L}{A}$$


e.g. find resistivity ρ .

Using the 0.1Ω wire above,

$$\rho = \frac{AR}{L} = \frac{10^{-4} \text{ m}^2 \times 0.1 \Omega}{0.2 \text{ m}} = \underline{\hspace{2cm}} \Omega \text{ m}$$

Electromotive Force

Dr K M Hock

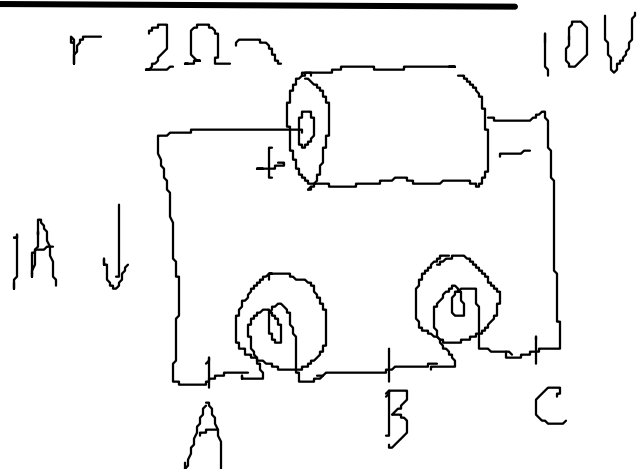

Recall potential difference p.d.
e.g. work done to bring unit charge from A to B.

e.g. Cell voltage is 10V. Is this p.d. between + and - poles?

No - because cell may have resistance r .
Part of the 10V must do work to bring charge thru' the cell itself.


The 10V is the work done to bring 1C of charge round the whole circuit.

↓
Electromotive force e.m.f. -

Work done to bring unit charge round the whole circuit.

e.m.f. versus p.d.

Dr K M Hock

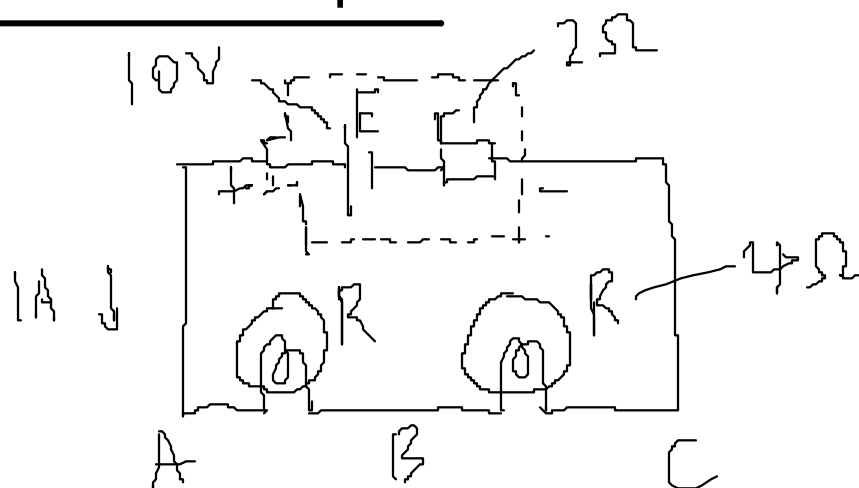

e.g. Find p.d. across AB.

$$V = IR = 1A \times 4\Omega = 4V$$

e.g. Find p.d. across AC

Since 2 light bulbs have same R,
 2x work done on 1C from A to C is
 2x " " from A to B.

$$\text{So answer} = 2 \times 4V = 8V$$

e.g. Find voltage across +, - poles.


10V? X charge from + to - flows from A to C. So answer is 8V.

Why not 10V??

show an understanding of the effects of the internal resistance of a source of e.m.f. on the terminal potential difference and output power.

Internal Resistance

Dr K M Hock

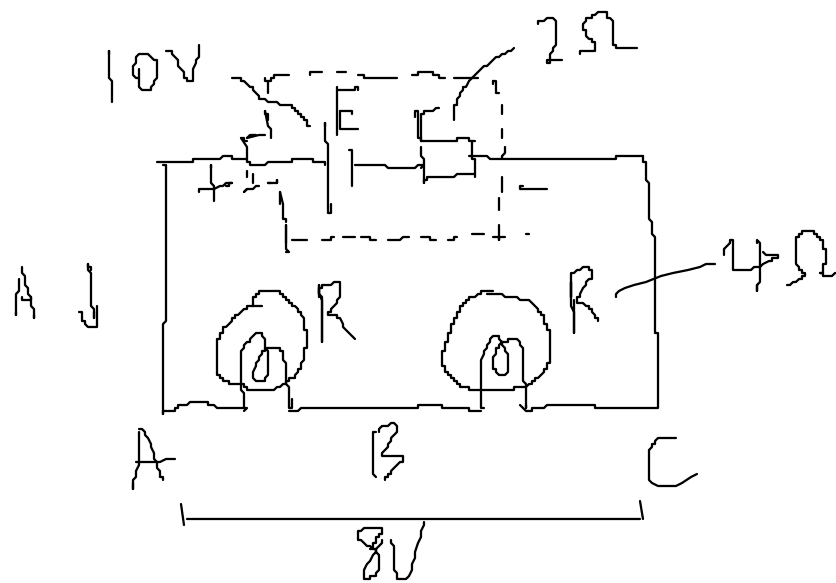

e.g. $8V$ across AC


→ $8J$ to bring $1C$ from A to C.

$10V$ e.m.f.

→ $10J$ to bring $1C$ round whole circuit.

The difference?

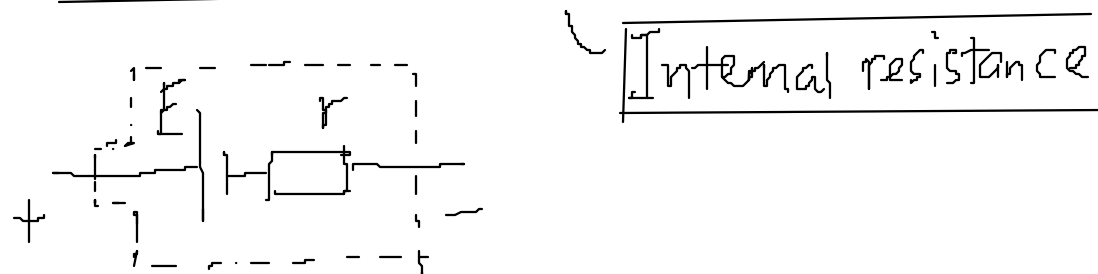→ $2J$ to bring $1C$ thru'
cell's own resistance r



e.g. What if I remove the circuit?

What is the terminal p.d. now?

across +, -

Ans. $10V$, ∵ no work thru' r .