


show an understanding and use the terms period, frequency, peak value and root-mean-square value as applied to an alternating current or voltage

Alternating Current




Dr K M Hock

Current that keeps changing direction.

flipping the cell

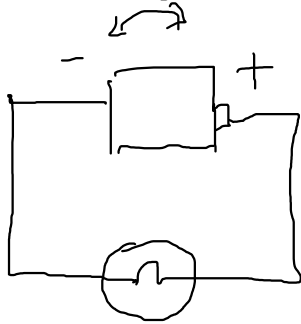

generator

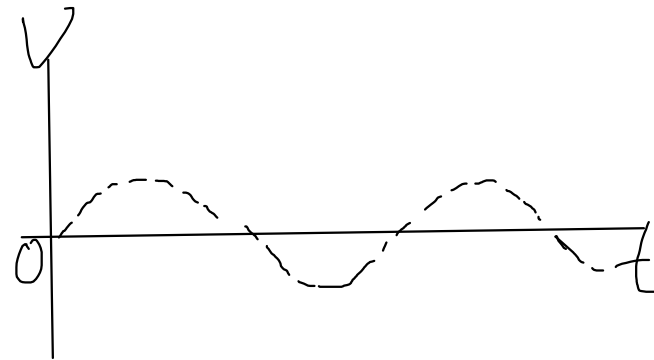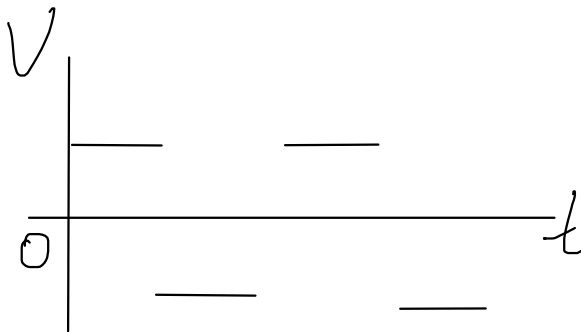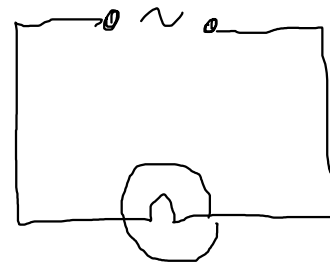

e.g. main electricity








frequency = no. of cycles per unit time

show an understanding and use the terms period, frequency, peak value and root-mean-square value as applied to an alternating current or voltage

Root-mean-square

Dr K M Hock

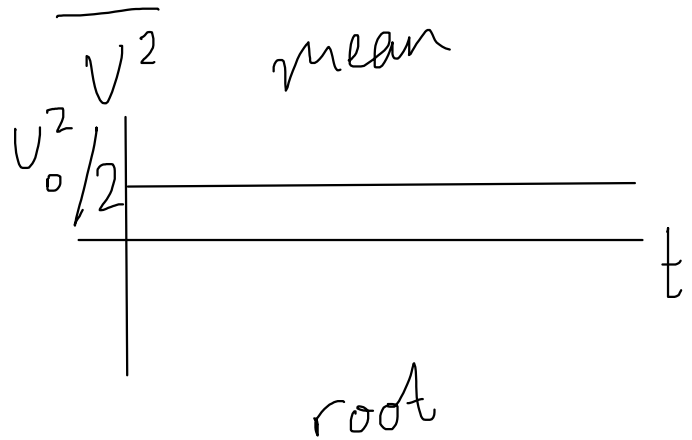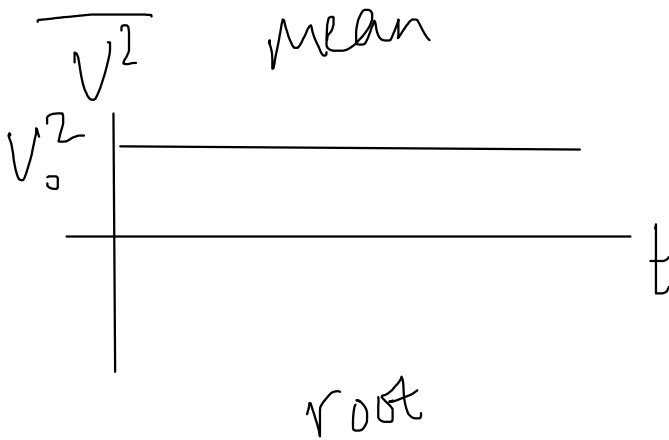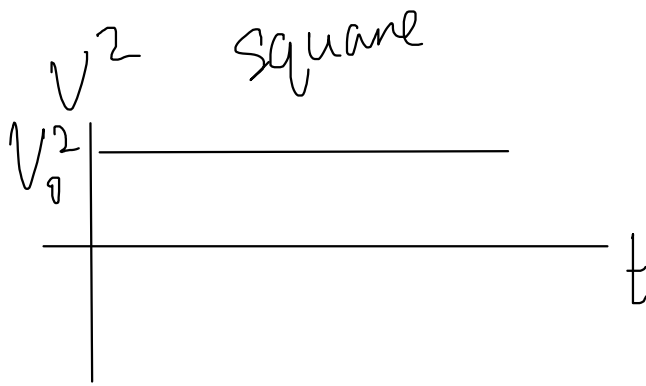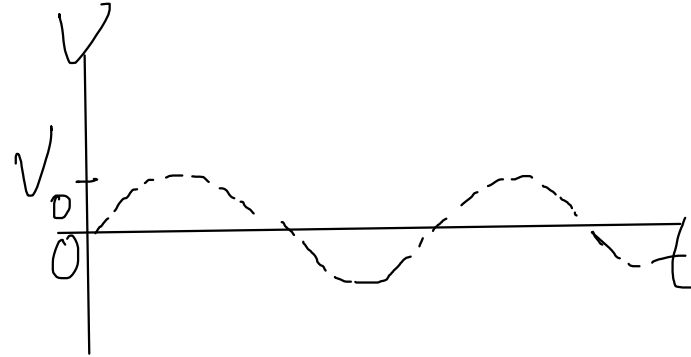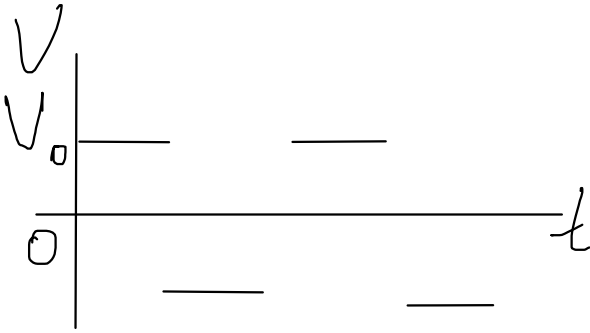

$$\sqrt{V_0^2} = V_0$$



$$\sqrt{\frac{V_0^2}{2}} = \frac{V_0}{\sqrt{2}}$$

root - mean - square (rms)



deduce that the mean power in a resistive load is half the maximum power for a sinusoidal alternating current

Mean Power

Dr K M Hock

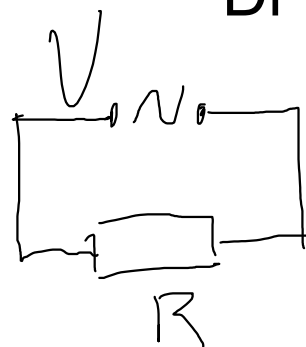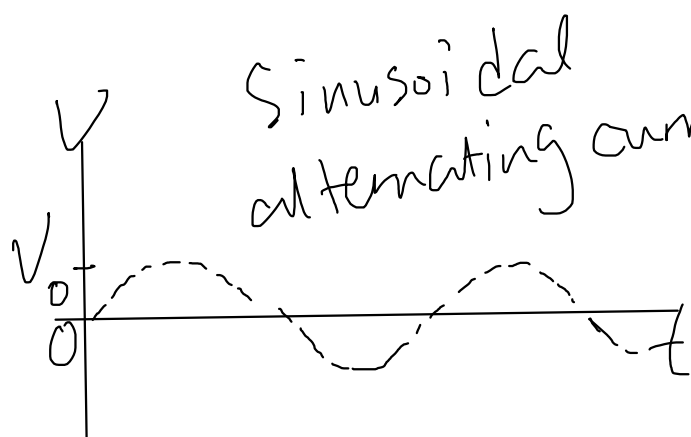

$$\text{Power} = \frac{V^2}{R}$$

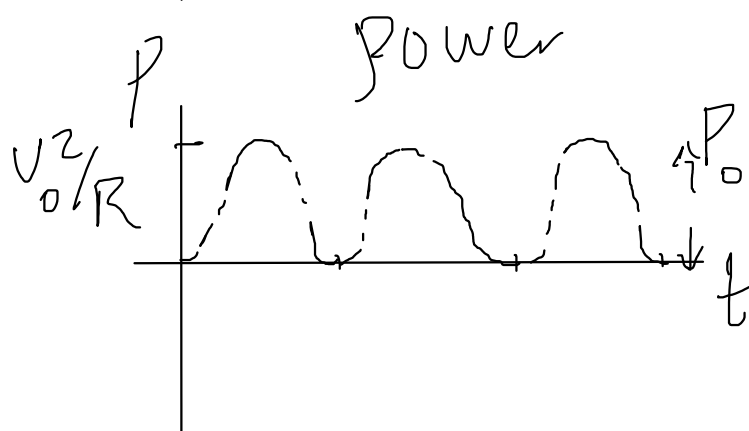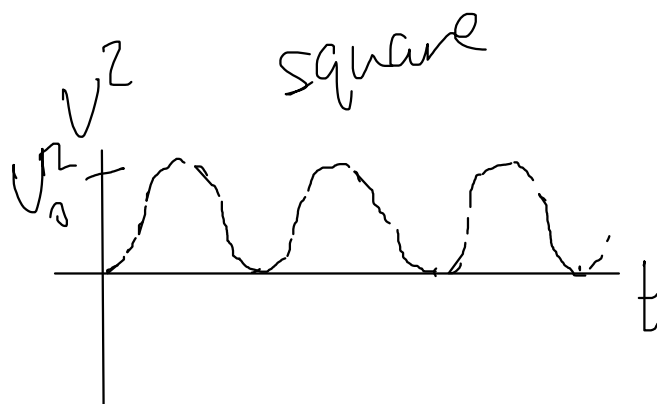

Mean power



$$\bar{P} = \frac{1}{2} P_0$$

represent an alternating current or an alternating voltage by an equation of the form $x = x_0 \sin \omega t$


a. c. equation

Dr K M Hock

Examples:

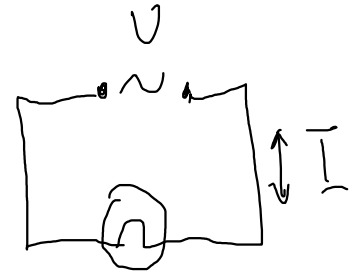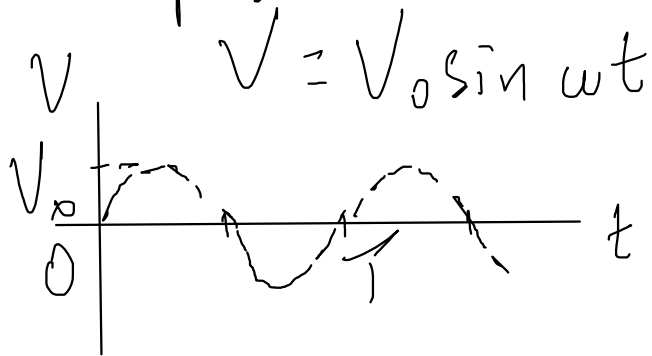

$$\omega = \frac{2\pi}{T}$$

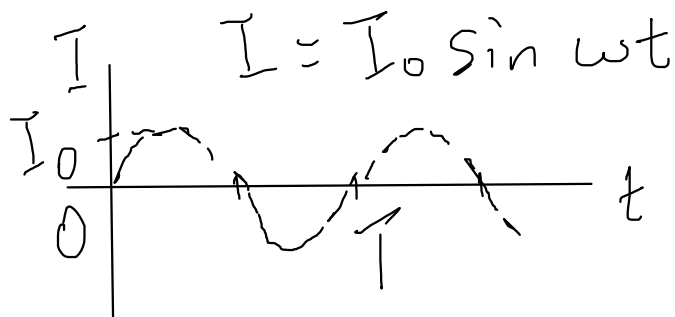


frequency f :

$$f = \frac{1}{T}$$

$$\omega = 2\pi f$$




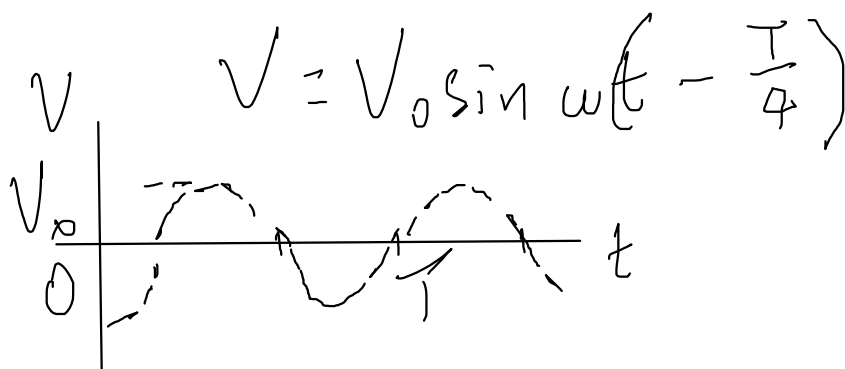
Can also start at other time of the cycle, e.g.,



distinguish between r.m.s. and peak values and recall and solve problems using the relationship $I_{rms} = I_0 / \sqrt{2}$ for the sinusoidal case

r.m.s. and peak values

Dr K M Hock

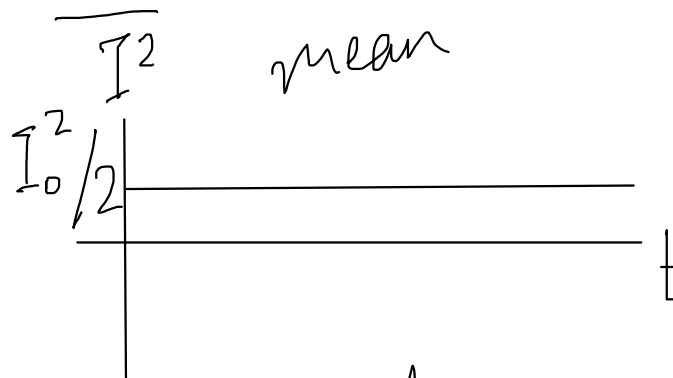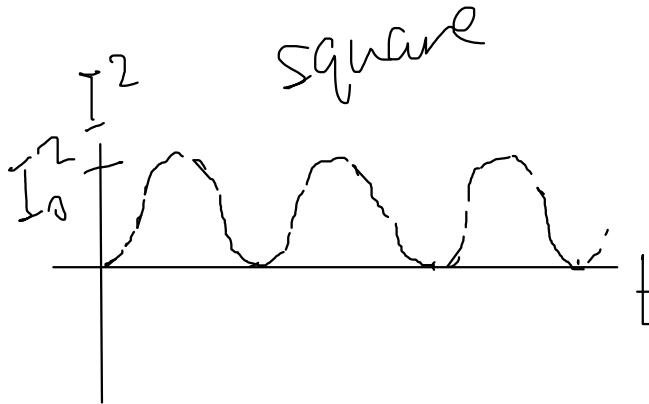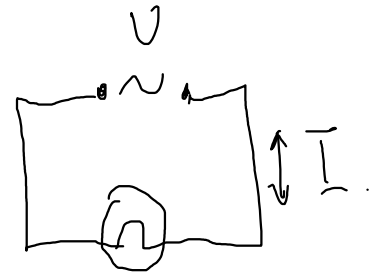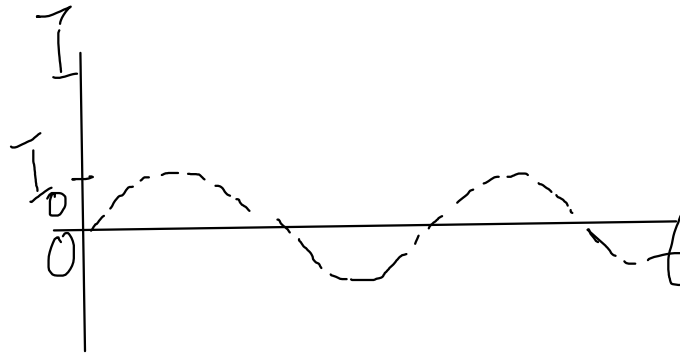

a kind of average


root

rms value = $\sqrt{\overline{I^2}} = \frac{I_0}{\sqrt{2}}$ peak value

show an understanding of the principle of operation of a simple iron-cored transformer and recall and solve problems using $N_s / N_p = V_s / V_p = I_p / I_s$ for an ideal transformer

Transformer

Dr K M Hock

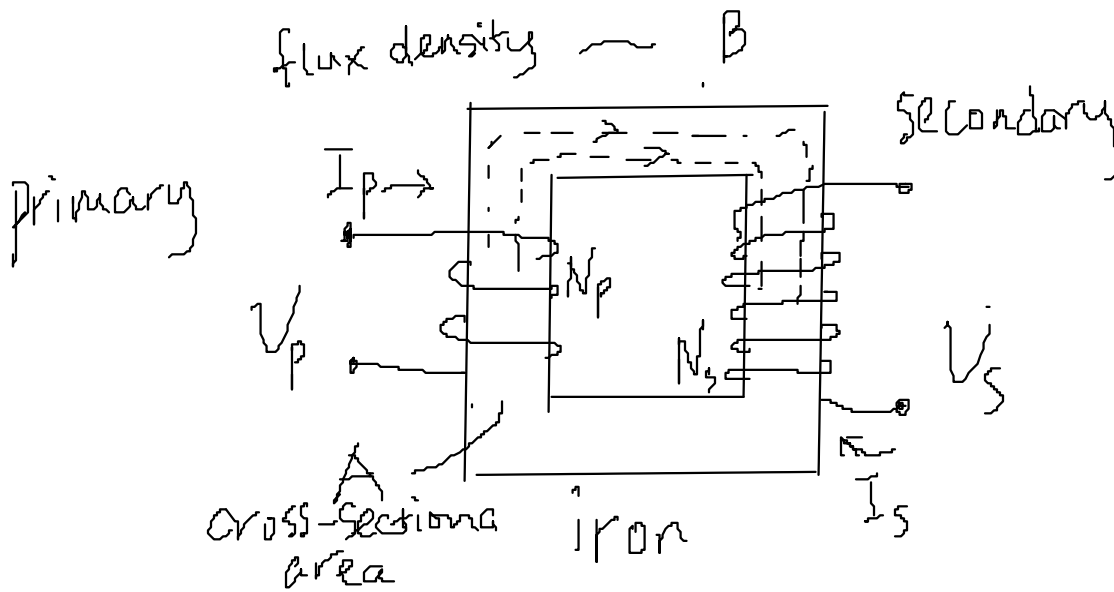

Flux thru' both primary and secondary coil
 Core equal : $\Phi = BA$.

Faraday's law :

primary coil

$$V_p = -N_p \frac{d\Phi}{dt}$$

secondary "

$$V_s = -N_s \frac{d\Phi}{dt}$$

Dividing :

$$\boxed{\frac{V_p}{V_s} = \frac{N_p}{N_s}}$$

Assume no heat loss in iron core :

power in power out


$$\boxed{V_p I_p = V_s I_s}$$

→ good for long distance transmission


explain the use of a single diode for the half-wave rectification of an alternating current.

Convert a.c. to d.c.

Dr K M Hock

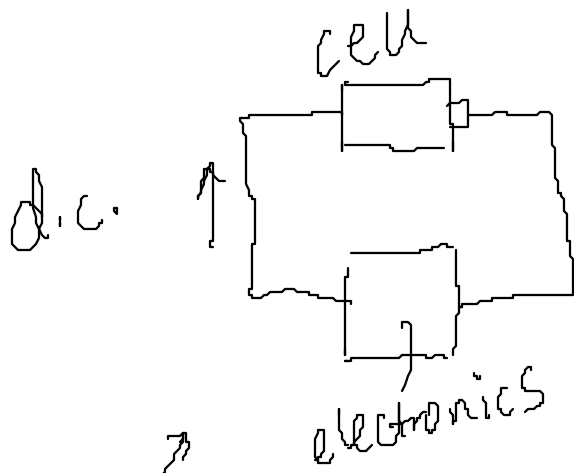


low power

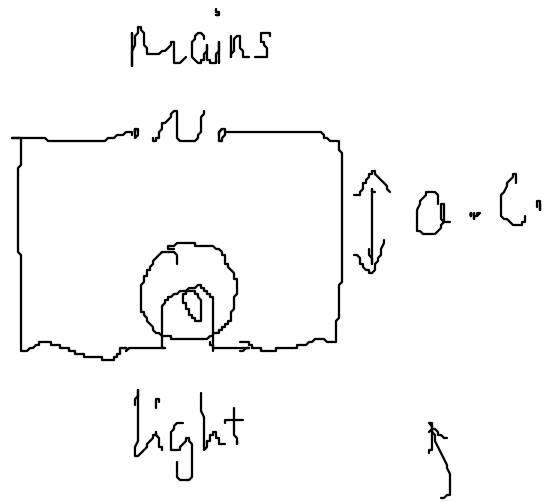


not good for electronics

How to convert a.c. to d.c. ?

e.g. just add a diode.

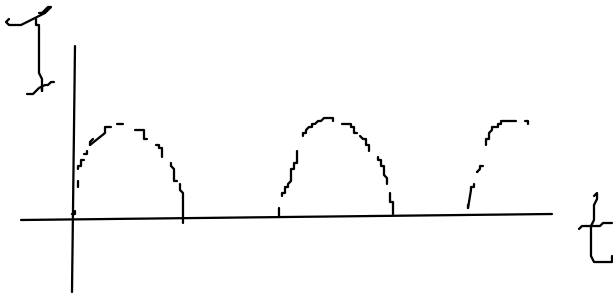

only one direction allowed by diode →

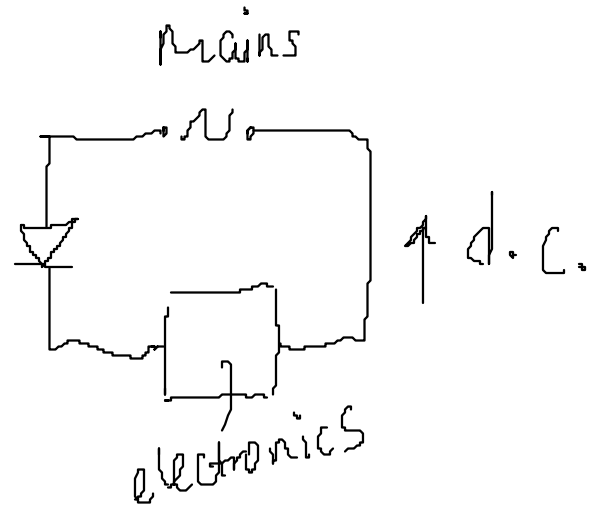

half wave rectification