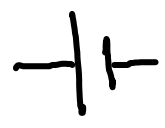


draw circuit diagrams with power sources (cell or battery), switches, lamps, resistors (fixed and variable), fuses, ammeters and voltmeters, bells, light-dependent resistors, thermistors and light-emitting diodes


# Circuit Symbols

Dr K M Hock


cell



battery

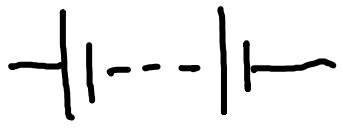

switch

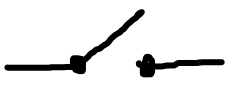


lamp



resistor (fixed)



Variable resistor

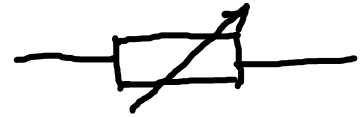

fuses



ammeters




voltmeters



bells



light-dependent resistors

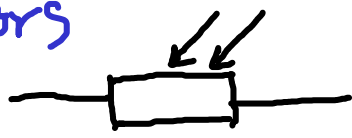

thermistors



diode



light-emitting diode




state that the current at every point in a series circuit is the same and apply the principle to new situations or to solve related problems
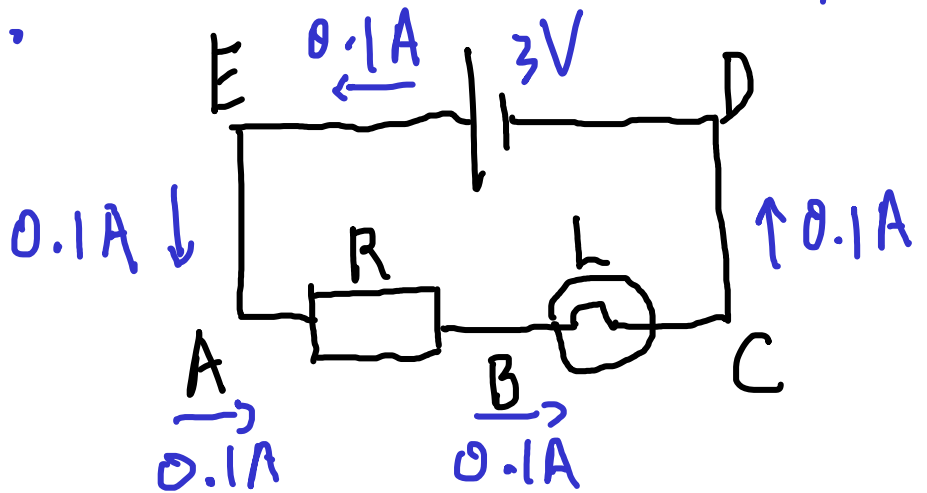
## Current in Series Circuit

Dr K M Hock

e.g. If all things in a circuit are connected one after another, they are in series.




Then current at any point - A, B, C, ... - must be the same.

What if they are not?

e.g. like this -

0.2A goes into lamp L and 0.1A comes out

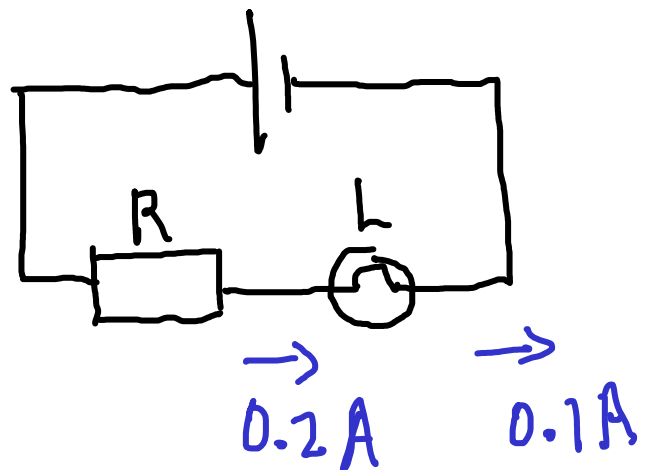


Then 0.1C must accumulate in L every 1s.  
- never been observed.

state that the sum of the potential differences in a series circuit is equal to the potential difference across the whole circuit and apply the principle to new situations or to solve related problems

## p.d. in series

Dr K M Hock

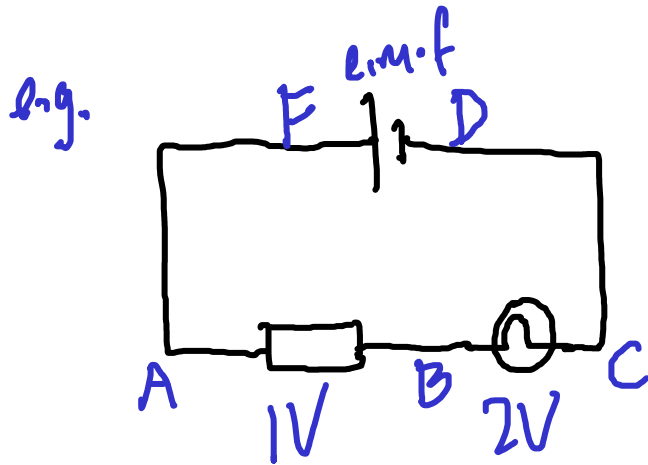

How much work is done to bring 1C of charge from

- (i) A to B
- (ii) B to C
- (iii) C to D
- (iv) D to F ?

Answers. Using  $V = \frac{W}{Q} \rightarrow W = QV$ ,

- (i) 1J (ii) 2J (iii) 0J (iv) 0J

e.g. What is the p.d. across AC?

Ans. Since p.d. is work for 1C, can just add:

$$\begin{aligned} \text{p.d. AC} &= \text{p.d. AB} + \text{p.d. BC} \\ &= 1V + 2V = 3V \end{aligned}$$

e.g. What is the e.m.f. of the cell?

Ans. Since all work is done by the cell, so

e.m.f. = sum of p.d.'s of all parts of circuit (in series)

$$(V = V_1 + V_2) = 1V + 2V = 3V.$$


state that the current from the source is the sum of the currents in the separate branches of a parallel circuit and apply the principle to new situations or to solve related problems

## Currents in Parallel

Dr K M Hock

e.g. The circuit branches into 2 wires at A and joins back at B.

If  $I_2$  is  $0.2A$ , what is  $I_1$ ?

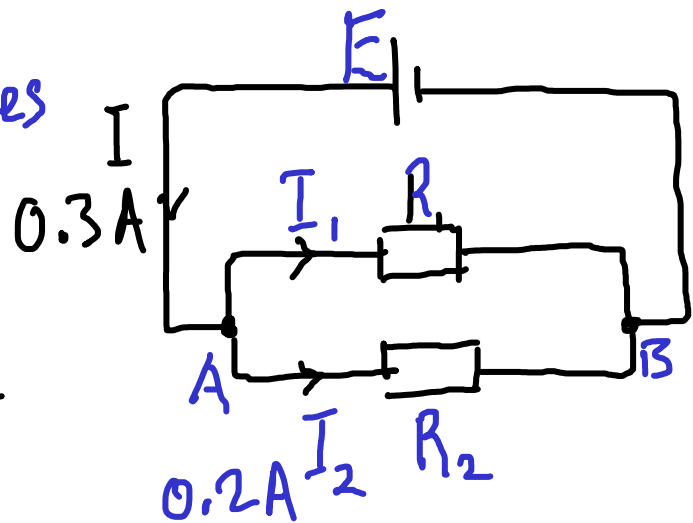

Ans.  $0.3C$  goes to  $A$  every  $1s$   
 $0.2C$  goes from  $A$  to  $R_2$  every  $1s$ .

Since charges do not collect at  $A$   
 $0.3 - 0.2 = 0.1C$  must go from  $A$  to  $R_1$  in  $1s$ .

$\therefore$  current  $I_1 = I - I_2 = 0.1A$ .

---

Current from the source  
= Sum of currents in  
separate branches of  
a parallel circuit

e.g. cell

e.g.


$$I = I_1 + I_2$$

state that the potential difference across the separate branches of a parallel circuit is the same and apply the principle to new situations or to solve related problems

## p.d. in parallel

Dr K M Hock

e.g.

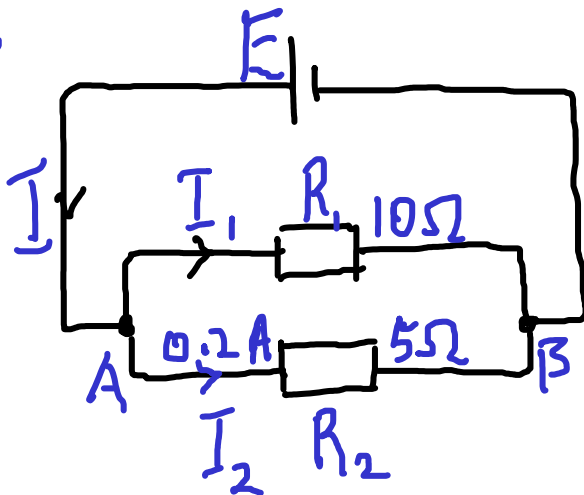

Find

- (i) p.d. across  $AB$
- (ii)  $I_1$
- (iii)  $I$
- (iv)  $E$  (e.m.f.)

Answers.

(i)  $(V = IR)$  p.d.  $AB =$  p.d. across  $R_2$   
 $= 0.2 \times 5 = 1V.$

(ii)  $(I = \frac{V}{R})$  p.d. across  $R_1 =$  p.d.  $AB$   
 In  $R_1$ ,  $I_1 = \frac{1V}{10\Omega} = 0.1A$

(iii)  $I = I_1 + I_2 = 0.1 + 0.2 = 0.3A$

(iv)  $E =$  p.d.  $AB = 1V$


---

p.d. across separate branches of parallel circuit is the SAME. e.g.  $R_1, R_2$  above

recall and apply the relevant relationships, including  $R = V/I$  and those for current, potential differences and resistors in series and in parallel circuits, in calculations involving a whole circuit

# Circuit Calculations

Dr K M Hock

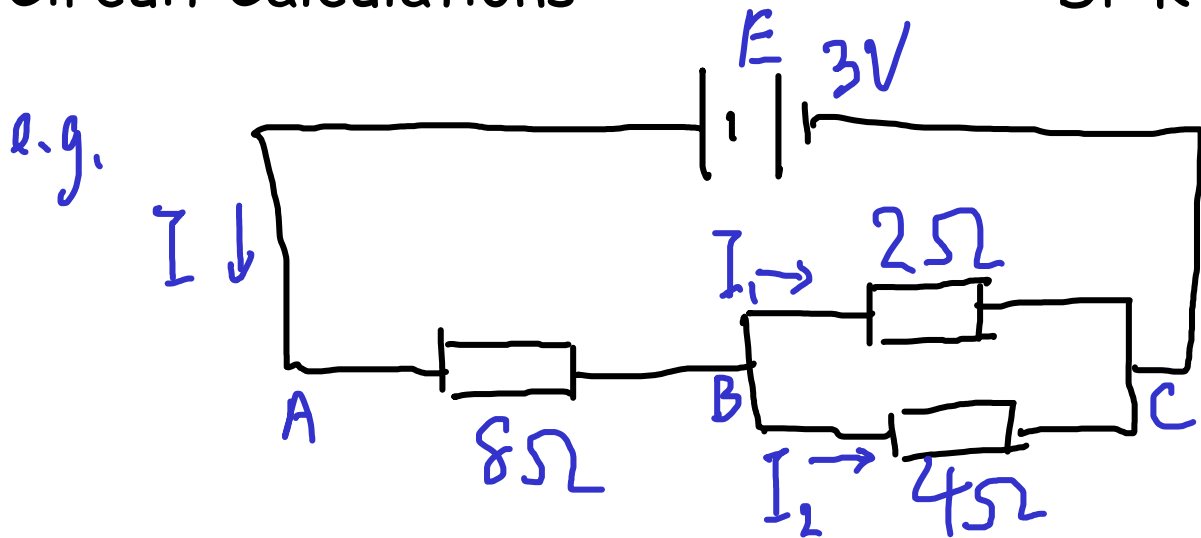

- Find
- (i) effective resistance between B, C
  - (ii) " " " "
  - (iii)  $I$
  - (iv) p.d. across AB
  - (v) p.d. across BC
  - (vi)  $I_1$
  - (vii)  $I_2$

Answers. (i)  $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$   
 $\frac{1}{R} = \frac{1}{2} + \frac{1}{4} = \frac{3}{4} \rightarrow R = \frac{4}{3} \Omega$

(ii)  $R = R_1 + R_2 = 8 + \frac{4}{3} = 9\frac{1}{3} \Omega$

(iii)  $I = \frac{V}{R} = \frac{3}{9\frac{1}{3}} = \frac{9}{28} A$

(iv)  $V = IR = \frac{9}{28} \times 8 = \frac{18}{7} V$

(v) ( $V = V_1 + V_2$ ) p.d. BC = e.m.f. - p.d. AB  
 $= 3 - \frac{18}{7} = \frac{3}{7} V$


(vi)  $I_1 = \frac{V}{R_1} = \frac{3/7}{2} = \frac{3}{14} A$  (vii)  $I_2 = I - I_1 = \underline{\hspace{2cm}}$

## Potential Divider

Dr K M Hock

e.g. (i) Find the ratio  $V_1:V_2$ .  
 (ii) Then find  $V_1, V_2$

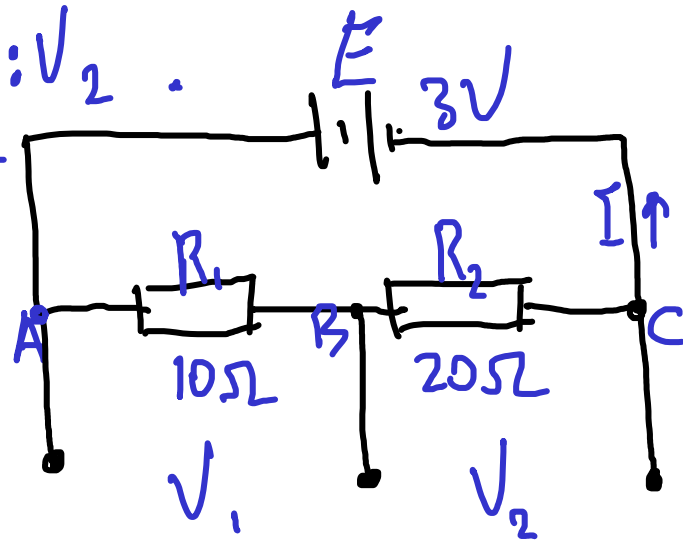Ans. (i)  $V_1 = IR_1$   
 $V_2 = IR_2$   
 $\frac{V_1}{V_2} = \frac{R_1}{R_2}$




$\therefore V_1:V_2 = R_1:R_2 = 10:20 = 1:2$

(ii) p.d. across AC = 3V =  $V_1 + V_2$

So 3V is divided in the ratio 1:2

$\therefore V_1 = 1V, V_2 = 2V$

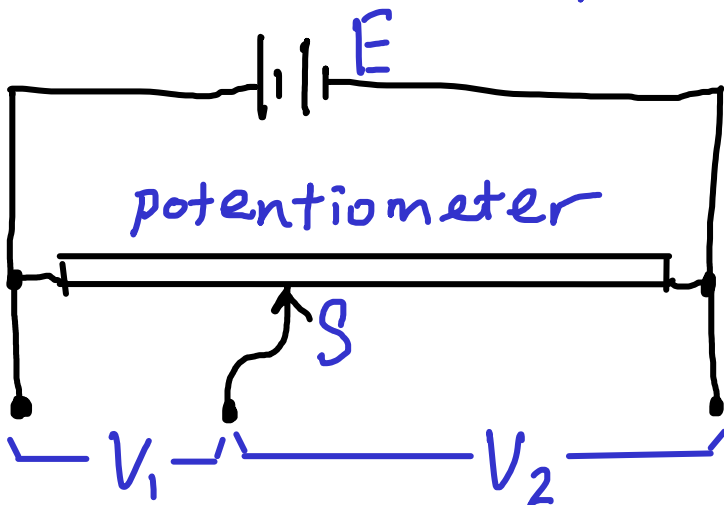Two resistors in series can divide a p.d. in the ratio  $R_1:R_2$ .



e.g. using a variable resistor like this, can adjust  $V_1$  by sliding contact S.


describe the action of thermistors and light-dependent resistors and explain their use as input transducers in potential dividers

## Thermistor and LDR

Dr K M Hock


Source  $E$  divided in the ratio  $V_1 : V_2 = R_1 : R_2$

e.g. fire alarm

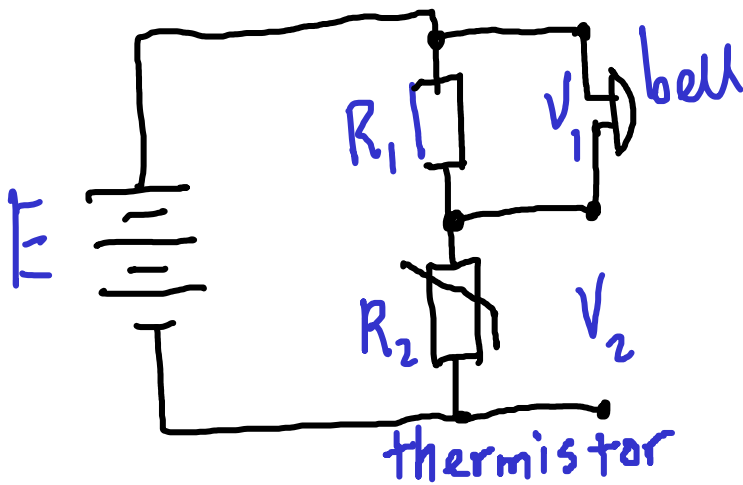

When hot,  $R_2 \downarrow$   
So  $V_2 \downarrow$   
and  $V_1 \uparrow$   
Then bell rings.

e.g. Street light

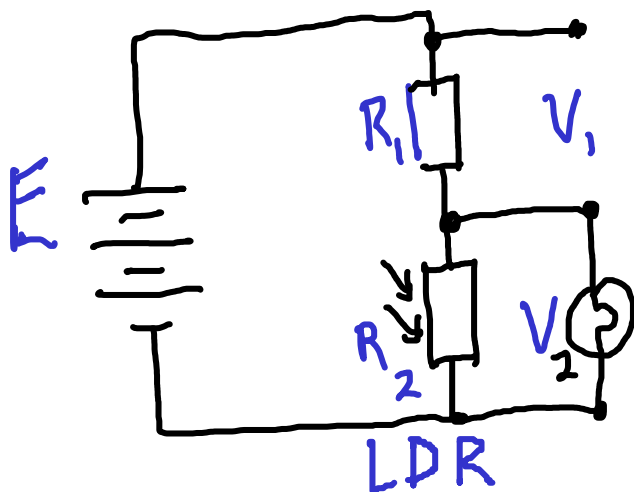

When dark,  $R_2 \uparrow$   
So  $V_2 \uparrow$   
Then lamp on.

Light Dependent Resistor




# Thermistor and LDR 2

Dr K M Hock

e.g. fire alarm. In a fire,  $R_2$  drops to  $1\Omega$ . Find the voltage  $V_1$  on the bell

room temperature

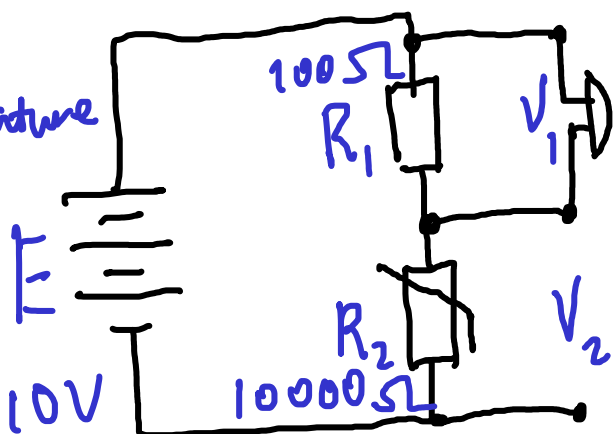


$V_1$  on the bell  
(i) before and  
(ii) after the fire.

(i)  $R_1 : R_2 = 1 : 10000$ .  $V_1 = \frac{1}{100+1} \times 10 \approx 0.1V$

(ii)  $R_1 : R_2 = 100 : 1$ .  $V_1 = \frac{100}{100+1} \times 10 \approx 9.9V$

e.g. Street light. At night,  $R_2$  increases to  $100'000\Omega$ .

daylight

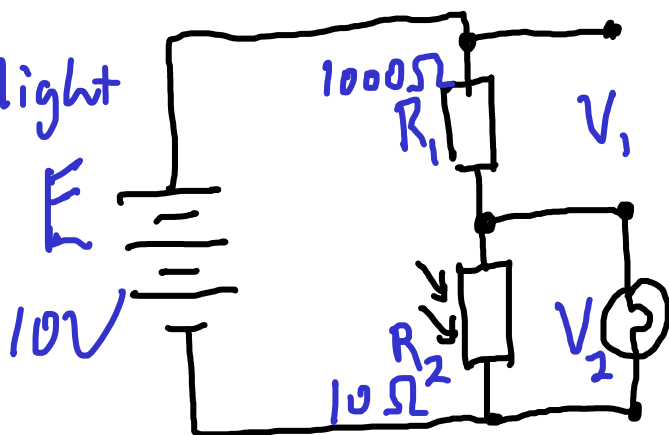

Find voltage  $V_2$  on the lamp

(i) in the morning and  
(ii) at night.

(i)  $R_1 : R_2 = 1000 : 10$ .  $V_2 = \frac{1}{1000+1} \times 10 \approx 0.1V$

(ii)  $R_1 : R_2 = 1000 : 100000$ .  $V_2 = \frac{1000}{1000+1} \times 10 \approx 9.9V$